


RGB LED DRIVER SHIELD FOR ARDUINO NANO

This is my second project for LED Driver based on CAT4101. First project was for single White LED, this projects has been designed to drive 3 channels RGB LED with PWM feature which helps to create multicolor LED light. Arduino Nano provided to generate PWM signal for RGB LED , also board has 3 tactile switches and Analog signal input to develop various RGB LED related applications. Each channel can drive Load up to 1A and input supply up to 12V DC. 1A X 3 Constant current LED driver shield for Arduino Nano has been designed for verity of LED related applications. The shield provides accurate LED current sink to regulate LED current in a string of LEDs or LED. The LED current is mirrored from the current flowing from the RSET Preset PR1. On board 2W X 3 LED is used for testing purpose. External LED or multiple LED string can be connected by pulling two wires from the PCB. The PCB has facility to mount Arduino Nano. Shield also has on board three tactile switches connected to Digital Pins D2,D3 and D12 using pull down resistor pack if required for any application. On board Trimmer potentiometer PR1, PR2, PR3 helps to set the maximum constant current. PWM input pin connected to Digital PWM pin D9, D10, and D11 of Arduino Nano to control the LED intensity. CN1 helps to power up the board, CN2 additional connector for Analog A6 input , 5V DC, GND and Reset for some Analog interface application.

Note: The project works with 12V Single supply Jumper J1 close to VIN. The board required dual supply for higher LED supply up to 24V, 7-12V for Nano and 24V separate for LED Driver CAT4101, in this case Jumper J1 is open.

Features


- Supply 7-12V DC (For Supply Input 24V refer Note)
- Load Current 1A Max
- Constant Current adjustable Up To 1A each Channel
- High Resolution PWM Dimming
- 3X On Board Trimmer Potentiometer to set the constant Current
- Nano Digital Pin D9,D10,D11 Connected to PWM of the CAT4101 IC
- Nano Digital Pin D2,D3,D12 Connected to Tactile Switch using Pull Down R-Pack
- When Trimmer Pots Minimum its set to 1A current, @ 1.5K Ohms set to 385mA
- CN1 Supply Input
- CN2 , Analog A6 Input and Reset Input
- J1 24V Supply or 12V Supply selection

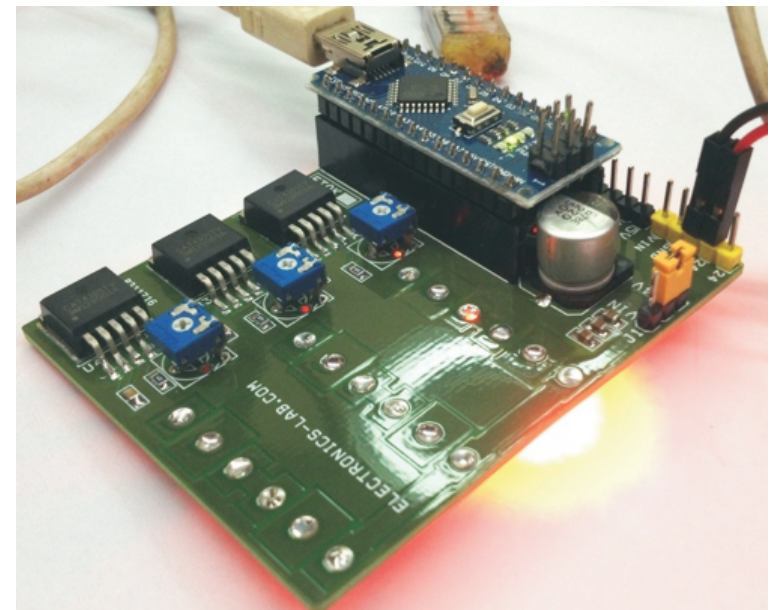


The board built using 3XCAT4101 IC from ON Semiconductor. The CAT4101 is a constant-current sink driving a string of high-brightness LEDs up to 1 A with very low dropout of 0.5 V at full load. It requires no inductor, provides a low noise operation and minimizes the number of components. The LED current is set by an external Trimmer preset PR1, PR2, PR3 connected to the RSET pin. The LED pin is compatible with high voltage up to 24 V, allowing the driving of long strings of LEDs. The device ensures an accurate and regulated current in the LEDs independent of supply and LED forward voltage variation. The PWM/EN input allows the device shutdown and the LED brightness adjustment by using an external pulse width modulation (PWM) signal coming from Arduino Nano D9, D10, and D11 pins. The driver features a thermal shutdown protection that becomes active whenever the die temperature exceeds 150°C.


PWM Duty Cycle and Frequency

Accurate linear dimming is compatible with PWM frequencies from 100 Hz to 5 kHz for PWM duty cycle down to 1%. PWM frequencies up to 50 kHz can be supported for duty cycles greater than 10%. When performing a combination of low frequencies and small duty cycles, the device may enter shutdown mode. This has no effect on the dimming accuracy, because the turn-on time T_{PS} is very short, in the range of 1s. To ensure that PWM pulses are recognized, pulse width low time T_{LO} should be longer than 1s. The CAT4101 enters a “zero current” shutdown mode after a 5 ms delay (typical) when EN/PWM is held low.

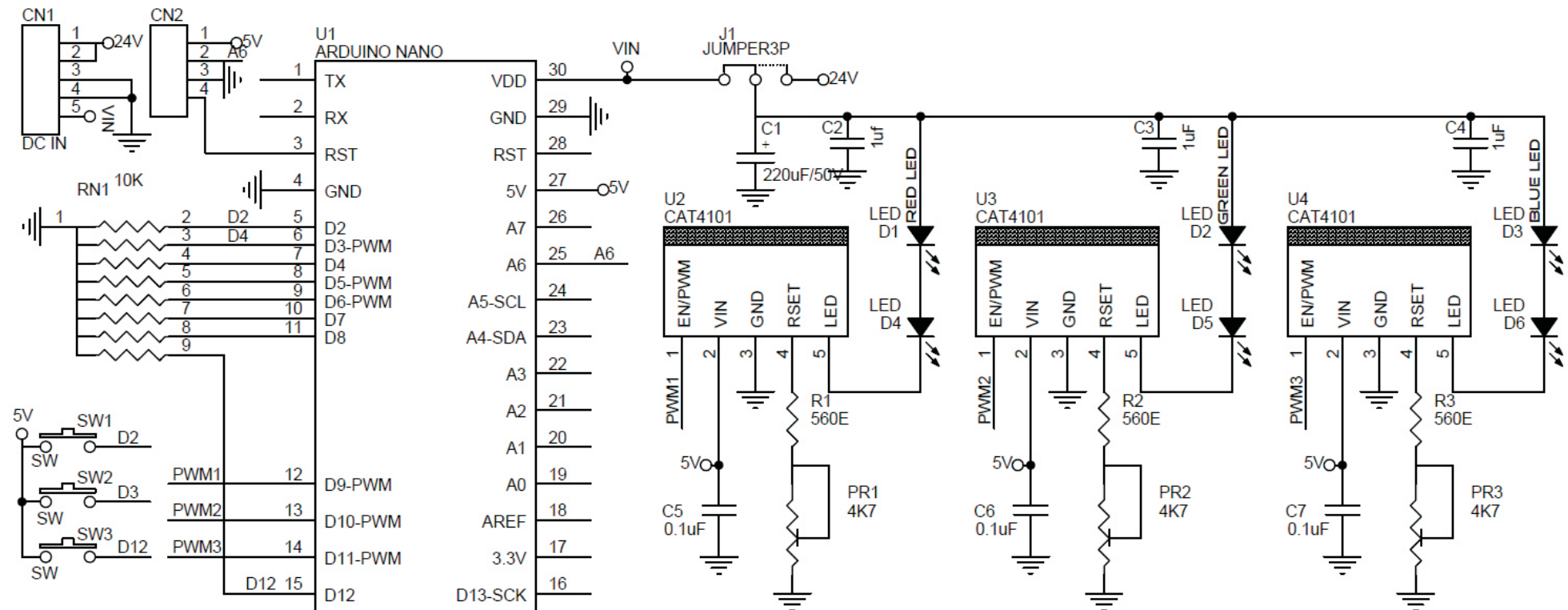


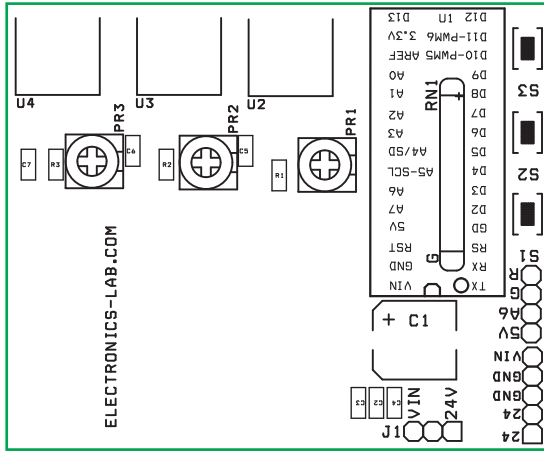


SILK SCREEN TOP

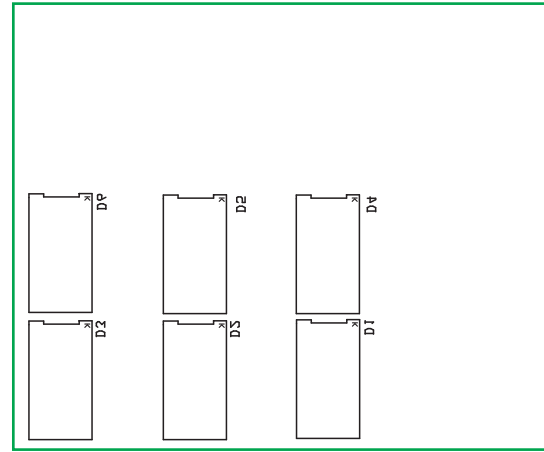

SILK SCREEN BOTTOM

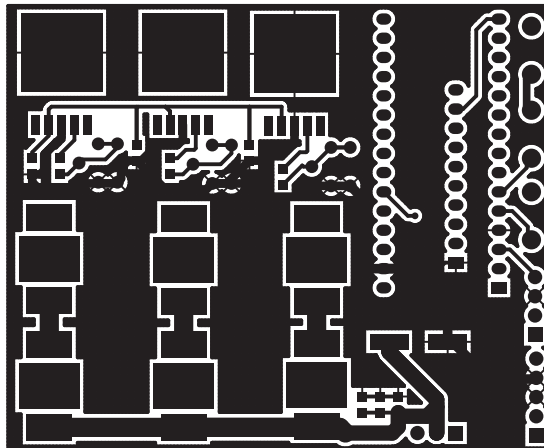

TOP

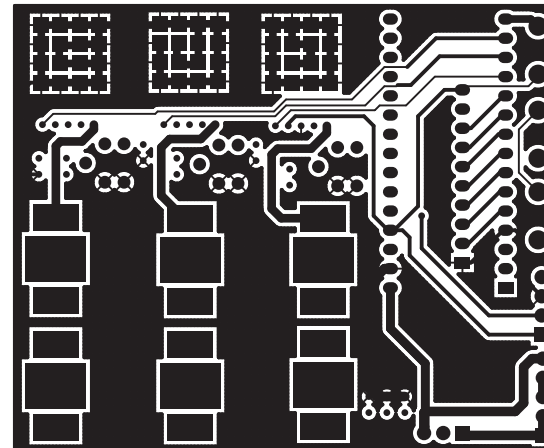

BOTTOM

BOM			
SR.	QNTY.	REF.	DESC.
1	1	CN1	5 PIN HEADER CONNECTOR
2	1	CN2	4 PIN HEADER CONNECTOR
3	1	C1	220uF/50V SMD
4	3	C2,C3,C4	1uF SMD 0805
5	3	C5,C6,C7	0.1uF
6	2	D1,D4	RED LED
7	2	D2,D5	GREEN LED
8	2	D3,D6	BLUE LED
9	1	J1	JUMPER & CLOSURE
10	3	PR1,PR2,PR3	4K7 TRIMMER POT
11	1	RN1	10K 9 PIN R PACK
12	3	R1,R2,R3	560E SMD 0805
13	3	SW1,SW2,SW3	2 PIN TACT SWITCH
14	1	U1	ARDUINO NANO
15	3	U2,U3,U4	CAT4101