

The LI-PO/LI-ON charger Arduino shield is mainly designed to power up the Arduino from single 3.6V LIPO battery. Li-Ion and Li-Pol Charger/ DC-DC Boost converter Arduino shield provides 6.5V/400mA from single Lithium Polymer battery. The Arduino shield is equipped with BQ21040 battery charger IC and CS5171 step up DC-DC converter. The shield also has proto area to utilize the maximum area of PCB. LIPO battery can be mounted on the same PCB. BQ21040 IC helps to charge 3.6V LIPO battery, Boost converter IC CS5171 converts 3.6V into approx. 6.5V to power up the Arduino. The CS5171 continues delivers current up to 400mA. Board required 5V DC to charge the battery. Charging current is set to 500mA. However it can be change as per requirement by altering R3 value, refer data sheet of BQ21040 for more information. LED D2 indicates when charging cycle is complete. On board NTC is to watch the over temperature of battery, recommended to keep the NTC sensor to keep close to battery while charging.

Features

- Charging Supply 5V/1A
- Charging Current 500ma
- Output Supply 6.5V/400mA
- Output Connected to VIN Pin of Arduino Shield.
- Compatible with single cell 3.6V LI-PO, LI-ON Battery
- Additional Proto-Area provided on PCB for development or to mount the Battery.
- PCB Dimensions 69.08MM X 51.58MM





BQ21040

The bq21040 is a highly integrated single cell Li-Ion and Li-Pol charger. The charger can be used to charge a battery, power a system or both. The charger has three phases of charging: Pre-charge to recover a fully discharged battery, fast-charge constant current to supply the buck charge safely and voltage regulation to safely reach full capacity. The charger is very flexible, allowing programming of the fast-charge current. This charger is designed to work with a USB connection or Adaptor (DC out). The charger also checks to see if a battery is present. The charger also comes with a full set of safety features: Temperature Sensing Standard, Over-Voltage Protection, DPM-IN, Safety Timers, and ISET short protection. All of these features and more are described in detail below. The charger is designed for a single power path from the input to the output to charge a single cell Li-Ion or Li-Pol battery pack. Upon application of a 5VDC power source the ISET and OUT short checks are performed to assure a proper charge cycle. If the battery voltage is below the LOWV threshold, the battery is considered discharged and a preconditioning cycle begins. The amount of the current goes into the battery during this phase is called pre-charge current. It is fixed to 20% of the fast charge current.


CS5171

The CS5171 IC is a 280 kHz switching regulators with a high efficiency, 1.5 A integrated switch. This IC operate over a wide input voltage range, from 2.7 V to 30 V. The flexibility of the design allows the chips to operate in most power supply configurations, including boost, flyback, forward, inverting, and SEPIC. The ICs utilize current mode architecture, which allows excellent load and line regulation, as well as a practical means for limiting current. Combining high frequency operation with a highly integrated regulator circuit results in an extremely compact power supply solution. The circuit design includes provisions for features such as frequency synchronization, shutdown, and feedback controls for either positive or negative voltage regulation.

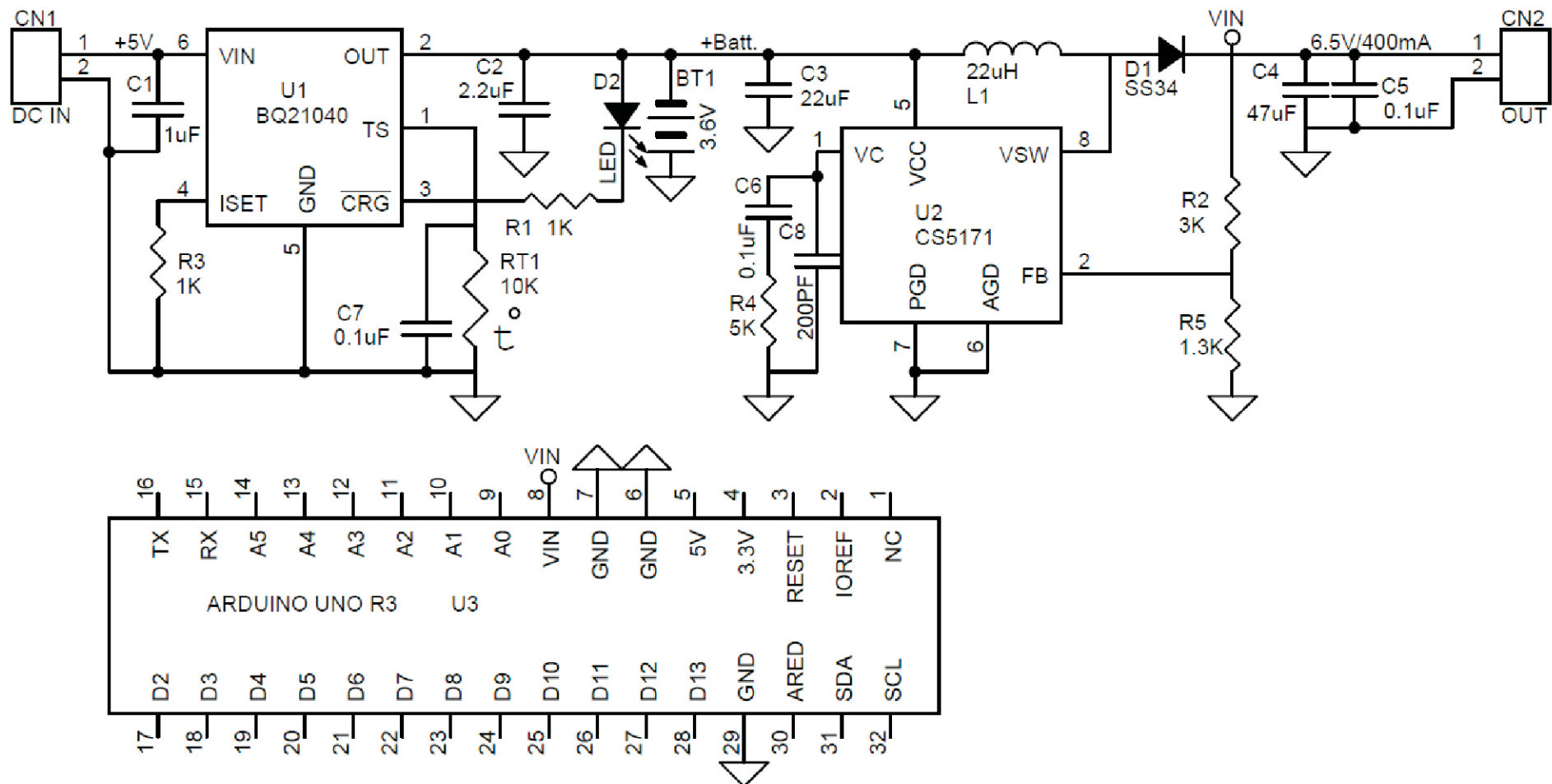


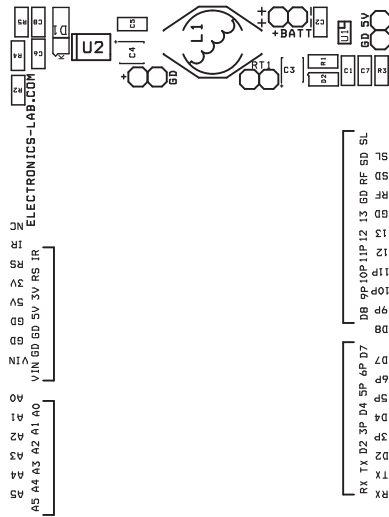

SILK SCREEN TOP

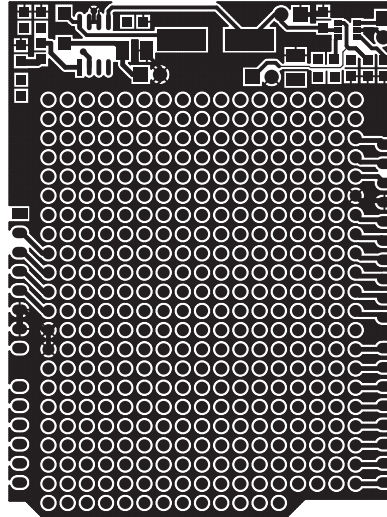

TOP LAYER

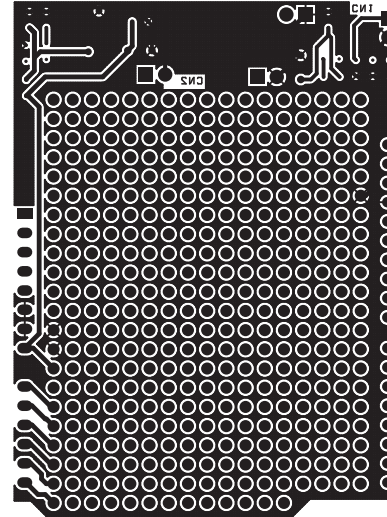

BOTTOM LAYER

PCB DIMENSIONS 69.08MM X 51.58

BOM			
SR.	QNTY.	REF.	DESC.
1	1	BT1	2 PIN HEADER CONNECTOR
2	1	CN1	2 PIN HEADER CONNECTOR
3	1	CN2	2 PIN HEADER CONNECTOR
4	1	C1	1uF 10V SMD 0805
5	1	C2	2.2uF 10V SMD 0805
6	1	C3	22uF SMD 1210
7	1	C4	47uF 10V SMD 1210
8	3	C5,C6,C7	0.1uF SMD 0805
9	1	C8	200PF SMD 0805
10	1	D1	SS34 SMD
11	1	D2	LED SMD 0805
12	1	L1	22uH SMD 12MM
13	1	RT1	10K NTC
14	2	R1,R3	1K SMD 0805
15	1	R2	3K SMD 0805 1%
16	1	R4	5K SMD 0805 1%
17	1	R5	1.3K SMD 0805 1%
18	1	U1	BQ21040 SMD SOT223-6
19	1	U2	CS5171 S08
20	1	U3	ARDUINO UNO R3 SHIELD

