

RGB LED Controller using Atmega328

This is a 3-channel, PWM based current-adjustable LED driver designed for RGB LED control. The circuit has been designed to control high current RGB LEDs or RGB LEDs strip. Colors of the three RGB LEDs can be set using 3 potentiometers, different colors are possible by adjusting these potentiometers.

RGB LED consists of 3 separate LEDs red, green, blue packaged in a single case. The RGB LEDs can emit different colors by mixing three basic colours.

We have used ATmega328 microcontroller to generate 3 PWM signals by reading analog inputs. These analog inputs are connected to 3 potentiometers. PWM outputs interfaced with gates of 3 x IRLR7843 MOSFETs which drive the high current loads. MC78M05 IC used to power the Atmega328 chip with 5V DC. The operating voltage of this circuit is 12V DC and each channel can drive a continuous load current up to 600mA or 1 A with cool air. Screw terminals provided for an easy connection for RGB LED strip or RGB LEDs. The circuit can drive 12V RGB strip/12V RGB LEDs. Any RGB LED strip with RGB and +V connection will work with this board or use a common anode RGB LED.


This project is built using an Atmega328 microcontroller which requires programming, example code can be found below. This example code is written using Arduino IDE, thus the Atmega328 chip requires boot-loader burning and code uploading. Follow this link to learn Atmega328 Chip programming and Boot-Loader burning.


<https://www.arduino.cc/en/Tutorial/BuiltInExamples/ArduinoToBreadboard>


Note: RGB LED without series resistor can be interfaced with this board, in this case, calculate the series resistors R4, R8, R12 values. The default value of these resistors is 0-Ohms.

Features

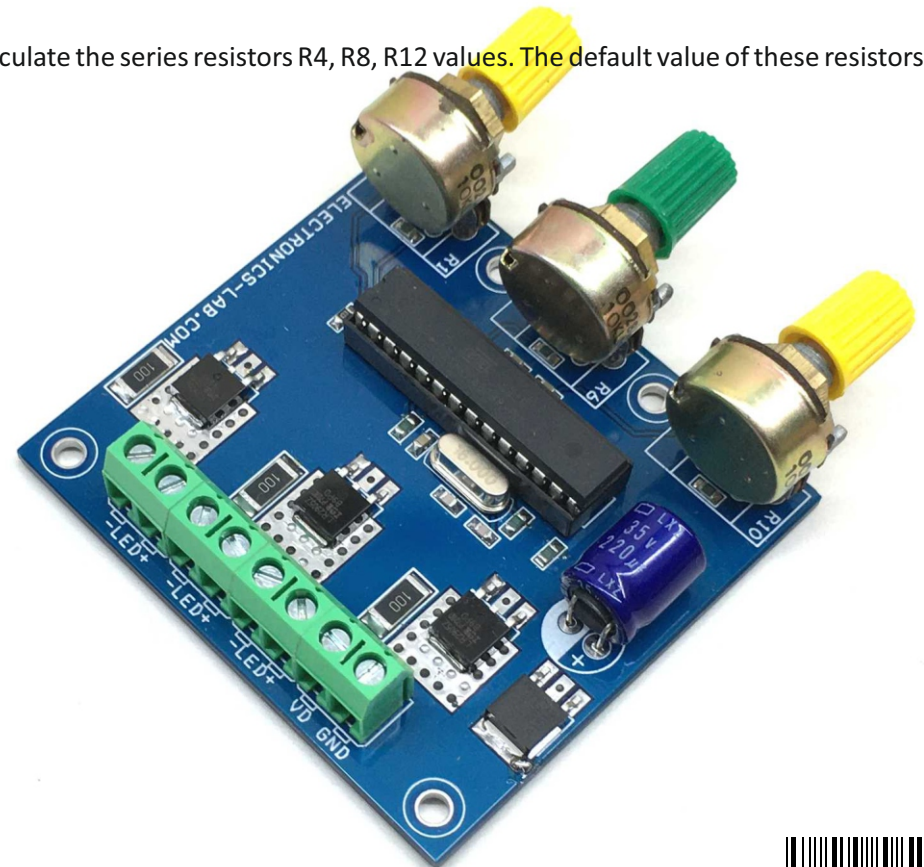
- Supply 12V DC (7V-15V)
- Load 600mA Each channel (1Amp with Fan)
- 3X Potentiometer to Adjust 3X LEDs
- PWM Duty Cycle Adjustable 0% to 100%
- Frequency 490/975 Hz
- Arduino Compatible Code
- PCB Dimensions 61MM X 67 MM



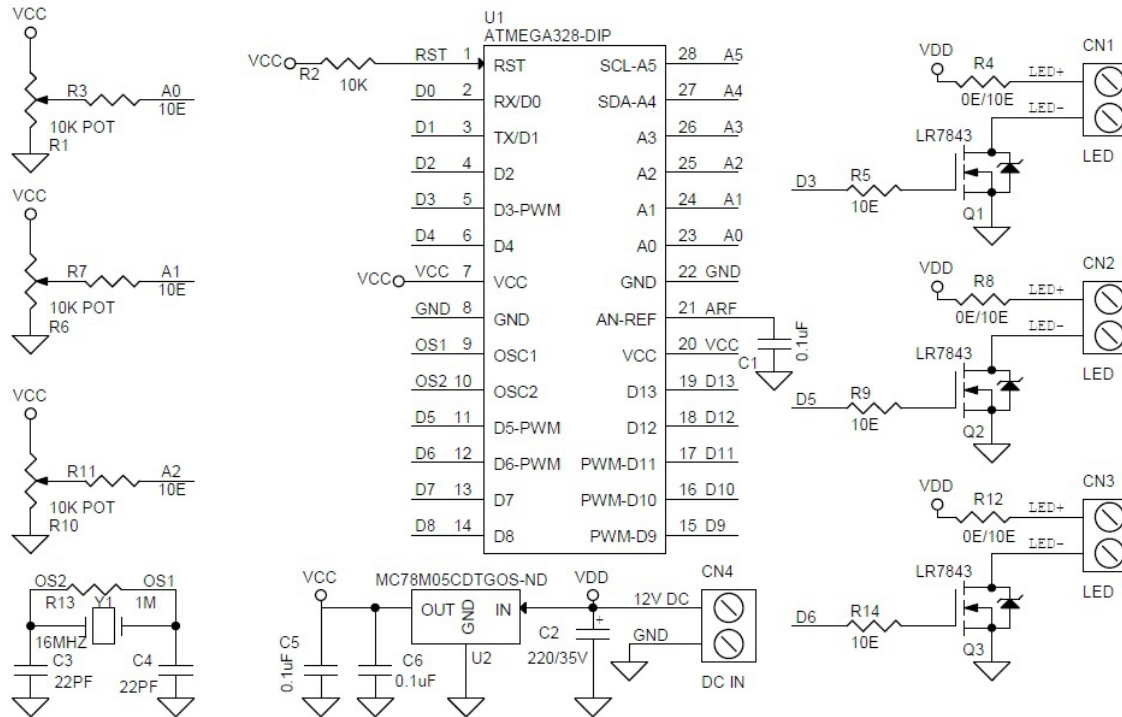


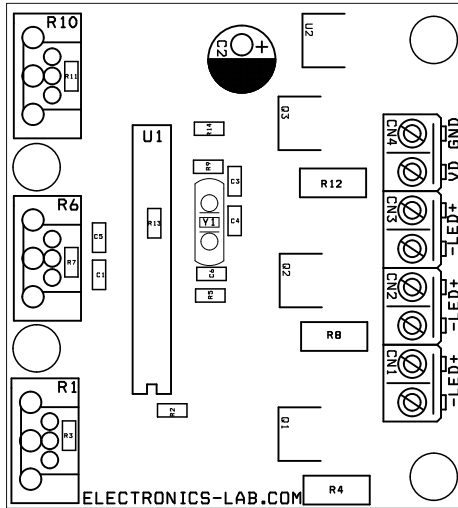

SILK SCREEN TOP

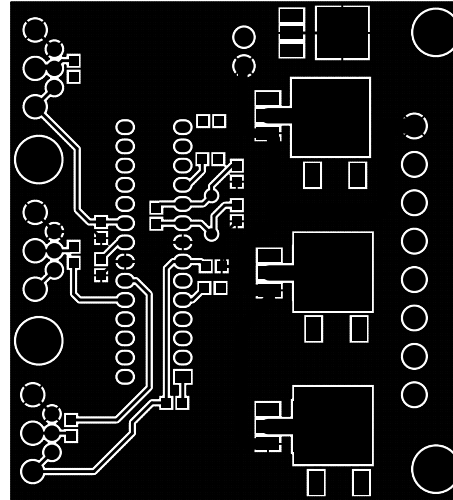


TOP LAYER

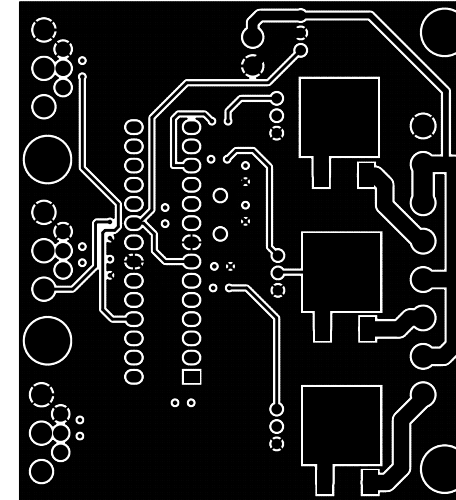

BOTTOM LAYER

PCB DIMENSIONS 61MM X 67MM

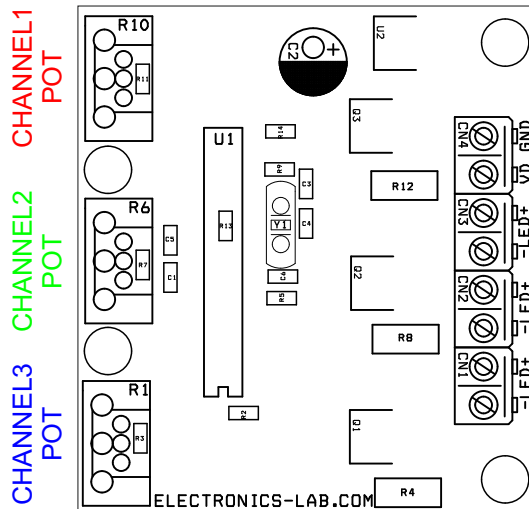

CHANNEL1 POT
CHANNEL2 POT
CHANNEL3 POT

GND
12V DC
+ LED1
- LED1
+ LED2
- LED2
+ LED3
- LED3

BOM				
SR	QNTY.	REF	DESC.	DIGIKEY/MOUSER
1	3	CN1,CN2,CN3	2 PIN SCREW TERMINLA	DIGIKEY-609-3918-ND
2	1	CN4	2 PIN SCREW TERMINLA	DIGIKEY-609-3918-ND
3	3	C1,C5,C6	0.1uF/50V SMD SIZE 0805	SIZE 0805
4	1	C2	220/35V	10MM RADIAL ELECTROLYTIC
5	2	C3,C4	22PF/50V SMD SIZE 0805	SIZE 0805
6	3	Q1,Q2,Q3	IRLR7843 MOSFET	DIGIKEY-IRLR2905ZTRPBFTR-ND
7	3	R1,R6,R10	10K POTENTIOMETER 16MM	DIGIKEY-987-1307-ND
8	1	R2	10K SMD RESISTOR SIZE 0805	5% SIZE 0805
9	6	R3,R5,R7,R9,R11,R14	10E SMD RESISTOR SIZE 0805	5% SIZE 0805
10	3	R4,R8,R12	0E OR 10E SMD RESISTOR SIZE 2512	5% SIZE 2512
11	1	R13	1M SMD RESISTOR SIZE 0805	5% SIZE 0805
12	1	U1	ATMEGA328-DIP	DIGIKEY-ATMEGA328P-PU-ND
13	1	U2	MC78M05CDTGOS-ND	DIGIKEY-MC78M05CDTGOS-ND
14	1	Y1	16MHZ CRYSTAL	DIGIKEY-X1103-ND
15	2	FEMALE -HEADER	14 PIN FEMALE HEADER PITCH 2.54MM	14 PIN FEMALE HEADER PITCH 2.54MM



