

Low Cost Room Thermometer Using 16X2 LCD, Atmega328 Chip

This is an easy to build small size and low-cost room thermometer. The project consists of LM35 analog temperature sensor, 16x2 LCD, and an Atmega328 chip. This compact board is Arduino compatible and provided with an onboard connector for Boot-Loader burning and Arduino IDE programming. Board also has 2 additional connectors for analog input and digital I/O. Trimmer potentiometer PR1 helps you to adjust the contrast of the LCD. Example Arduino Code for the thermometer is available as a download to test the board. The example will display the temperature value in Celsius as well as Fahrenheit. The operating voltage of the circuit is 5V DC and it draws approx. 35mA of current with backlight LED ON. Scale factor/Output of LM35 is 10mV/Centigrade. This board can also be used in other Arduino applications that require a 16x2 LCD and I/O Pins.

Features

Supply 5V DC Current Consumptions 35mA with LCD Backlite ON Temperature Measurement Range 0 to 110 Centigrade PCB Dimensions 41.43MM X 23.34MM

Arduino Pin configurations for Thermometer

LCD >>D12, D11, D5, D4, D3, D2 LM35 Temperature Sensor >> Analog Pin A1

Arduino Additional Pin Configurations

U3 >> VCC. Analog Pin A0. GND CN2 >> VCC, GND, Analog Pin A2, Digital PWM Pin D9 CN1 >> Arduino Programming



Bootloader Burning and Arduino Programming

Once you assemble the board and use a new ATmega328 chip, you'll need to burn the bootloader onto it. You can do this using an Arduino board as an in-system program (ISP). Follow the link below for more information on programming and bootloader burning Atmega328 chip.

https://www.arduino.cc/en/Tutorial/ArduinoToBreadboard

To burn the bootloader, follow these steps:

- Upload the ArduinoISP sketch onto your Arduino board. (You'll need to select the board and serial port from the Tools menu that correspond to your board.)
- Wire up the Arduino board and LCD microcontroller board as shown in the diagram.
- Select "Arduino UNO or Nano w/ ATmega328" from the Tools > Board menu.
- Select "Arduino as ISP" from Tools > Programmer
- Run Tools > Burn Bootloader

You should only need to burn the bootloader once. After you've done so, you can remove the jumper wires connected to pins 10, 11, 12, and 13 of the Arduino board. This board can be program using Arduino IDE with easy connection with Arduino UNO (without Micro-Controller on it) or FTDI USB to serial module.










The LM35 series are precision integrated-circuit temperature devices with an output voltage linearly-proportional to the Centigrade temperature. The LM35 device has an advantage over linear temperature sensors calibrated in Kelvin, as the user is not required to subtract a large constant voltage from the output to obtain convenient Centigrade scaling. The LM35 device does not require any external calibration or trimming to provide typical accuracies of \pm %°C at room temperature and \pm %°C over a full -55°C to 150°C temperature range. Lower cost is assured by trimming and calibration at the wafer level. The low-output impedance, linear output, and precise inherent calibration of the LM35 device makes interfacing to readout or control circuitry especially easy. The device is used with single power supplies, or with plus and minus supplies. As the LM35 device draws only 60 μ A from the supply, it has very low self-heating of less than 0.1°C in still air. The LM35 device is rated to operate over a -55°C to 150°C temperature range, while the LM35C device is rated for a -40°C to 110°C range (-10° with improved accuracy). The LM35-series devices are available packaged in hermetic TO transistor packages, while the LM35C, LM35CA, and LM35D devices are available in the plastic TO-92 transistor package.










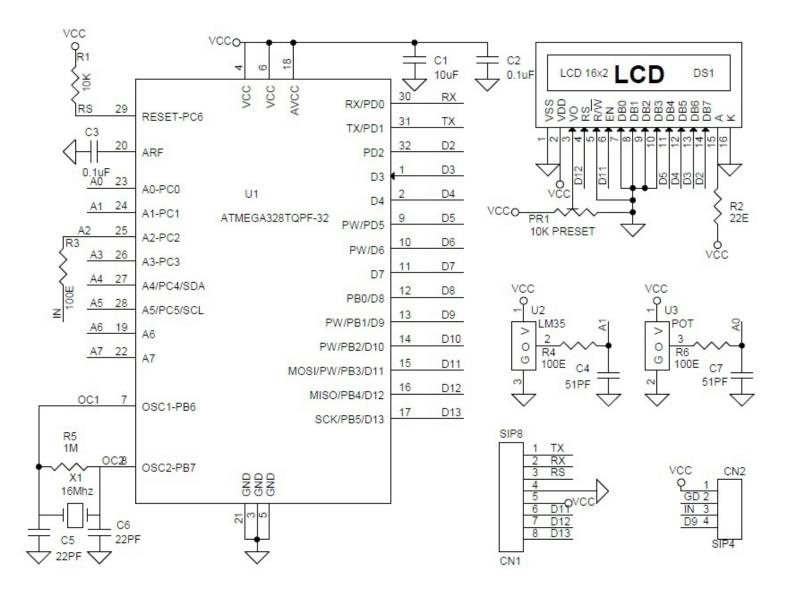










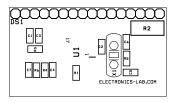

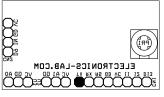

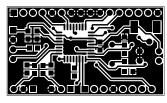

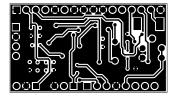


SILK SCREEN TOP

SILK SCREEN BOTTOM

TOP LAYER

BOTTOM LAYER

PCB DIMENSIONS 41.43MM X 23.34MM

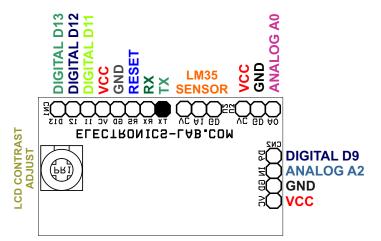

вом							
SR.	QNTY.	REF. DESC.					
1	1	CN1	8 PIN MALE HEADER 2.54 MM				
2	1	CN2	DNP				
3	1	C1	10uF/10V SMD 0805				
4	2	C2,C3	0.1uF/50V SMD 0805				
5	2	C4,C7	51PF SMD 0805 OPTIONAL				
6	2	C5,C6	22PF SMD 0805				
7	1	DS1	LCD 16x2				
8	1	PR1	10K PRESET				
9	1	R1	10K 5% SMD 0805				
10	1	R2	22E SMD 2510				
11	3	R3,R4,R6	100E SMD 0805				
12	1	R5	1M				
13	1	U1	ATMEGA328TQPF-32				
14	1	U2	LM35 TO92				
15	1	U3	DNP				
16	1	X1	16Mhz				

LCD 16X2


	\mathfrak{M}	mai	∞
C1 C3	17		R2
22	U1 ,	_ C2 C6	
C7 R6 R4 C4	R1		
	Ш	ELECTRONICS-LA	AB.COM









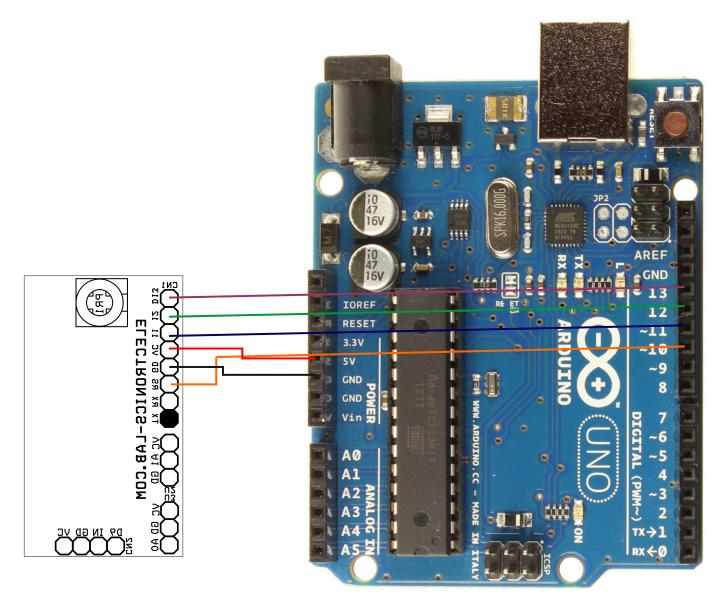


Burning the Bootloader Connections









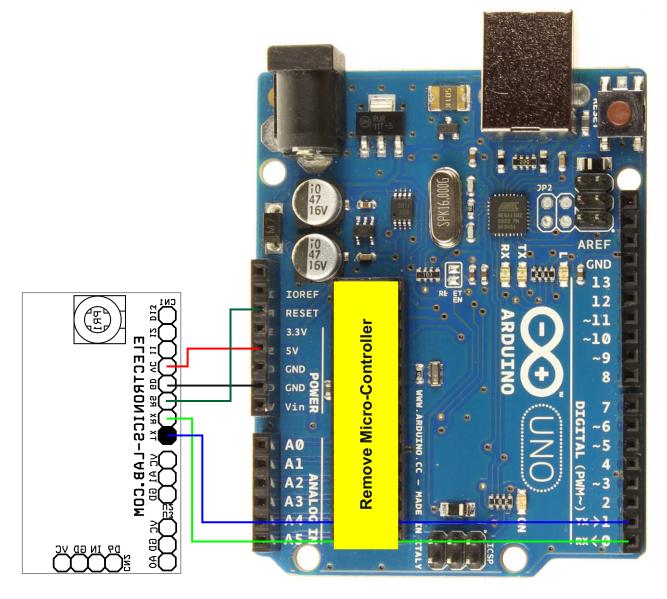

Arduino Programing Connections





