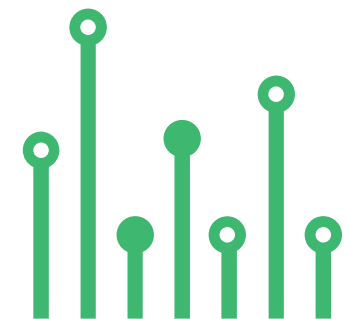


THE
electronics-lab
.com
**from ideas to
boards**

[electronics-lab - Projects](#) | [Embedded News](#) | [Online Community](#) | [e-Shop](#)

Open Source Hardware Electronics Projects

[electronics-lab.com /projects](https://electronics-lab.com/projects)





” Voltage to Current (V-I) Converter —



SKU: EL139515

Voltage to Current (V-I) Converter



The circuit shown here is a high-side voltage-to-current (V-I) converter. It translates an input voltage of 0 V to 2 V to an output current of 0 mA to 100 mA. The low offset voltage and offset drift of the OPA2333 facilitate excellent DC accuracy for the circuit.

The project provides a high-side current source that supplies an adjustable current to a ground reference load. The first op-amp stage sets a reference current based on the input control voltage. The second op-amp stage acts as a current mirror that gains the reference current and regulates the current sourced from the output PMOSFET Q2 to the load. R2, R4, and R10 set the output current based on the input control voltage. Components C7, R9, R8, R7, C6, R3 provide compensation to ensure stability of the circuit.



Note: Use high-precision, low-drift resistors for R2, R4, and R10 to minimize errors caused by resistor mismatch and temperature drift.

FEATURES

- Input Supply 5V DC
- Input Control Voltage 0 to 2V
- Output 0 to 100mA
- Jumper For External/Internal Control Voltage Selection
- Reference Voltage Generator Chip for 2V Control Voltage Source
- Header Connector for Input and Output and Power Supply
- On Board Power LED
- On Board Trimmer Potentiometer for Control Voltage Adjustment
- Header Connector for External Control Voltage
- PCB Dimensions 36.83 X 20.96MM



The V-I transfer function of the circuit is based on the relationship between the input voltage, V_{IN} , and the three current sensing resistors, R2, R4, and R10. The relationship between V_{IN} and R10 determines the current that flows through the first stage of the design. The current gain from the first stage to the second stage is based on the relationship between R2 and R4. The project is built using OPA2333. Low offset voltage, low-temperature drift, and rail-to-rail output are the key features of this op-amp. The OPA2333 CMOS operational amplifier is a high precision, 5- μ V offset, 0.05- μ V/ $^{\circ}$ C drift amplifier optimized for low-voltage, single-supply operation with an output swing to within 50 mV of the positive rail. The OPA2333 family uses chopping techniques to provide low initial offset voltage and near-zero drift over time and temperature. Low offset voltage and low drift reduce the offset error in the system, making these devices appropriate for precise DC control. The rail-to-rail output stage of the OPA2333 ensures that the output swing of the operational amplifier is able to fully control the gate of the MOSFET devices within the supply rails.

Control Voltage Input:

The project works with external or internal control voltage.


U1 REF5020 generates accurate 2V. Solder jumper J1 for internal control voltage, Trimmer potentiometer PR1 is provided to adjust the control voltage 0 to 2V.

For external control voltage input, open the jumper J1, CN1 provided to feed the external control voltage 2V, PR1 can be used to adjust the 0 to 2V.


Applications

- LED Drivers
- Optical Modules,
- Field Transmitters
- PLC Analog Output Modules

Schematic

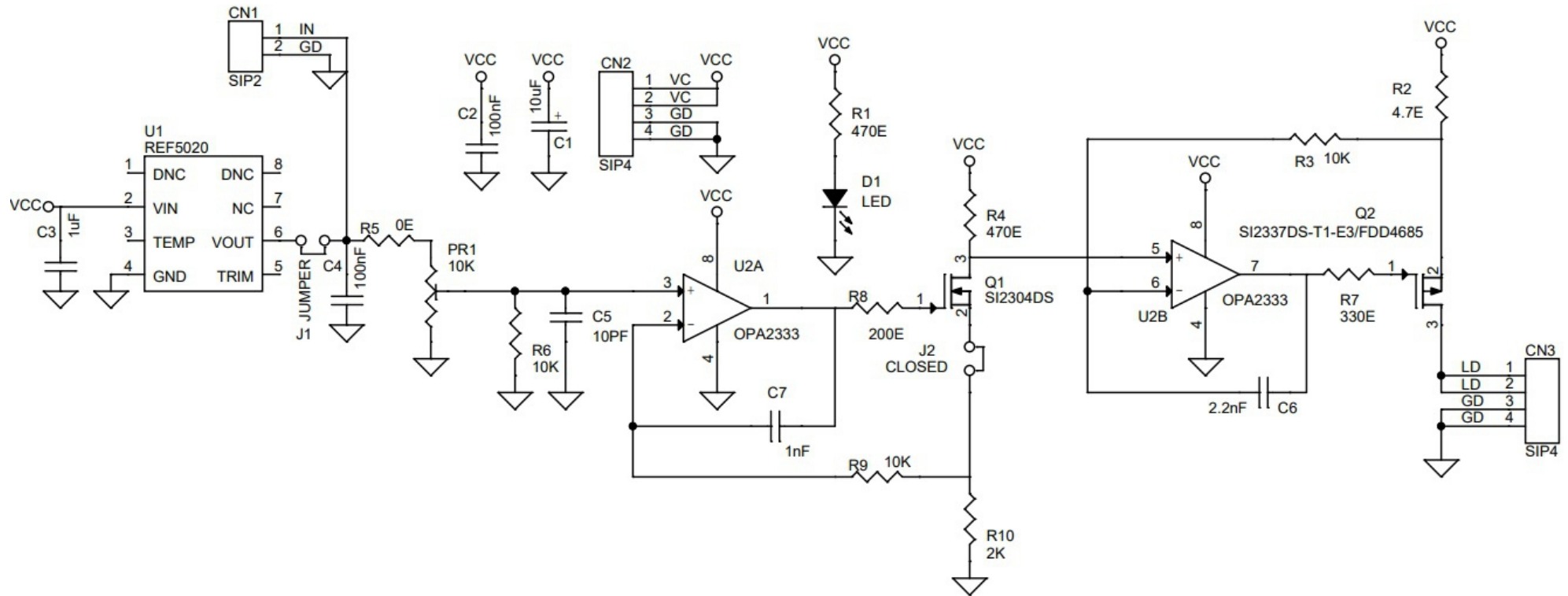




Connections

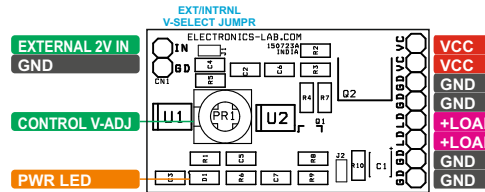


Connections and Other Details

- CN1: Pin 1 = 2V Input, Pin 2 = GND (External Control Voltage)
- CN2: Pin 1,2 = VCC, Pin 3,4 = GND
- CN3: Pin 1,2 = +Load, Pin 3,4 = GND
- D1: Power LED
- J1: Solder Jumper for External or Internal Control Voltage Selection.
Open = External Control Voltage, Closes = Internal Control Voltage
- J2: Always Closed


PCB

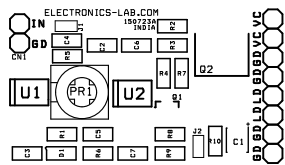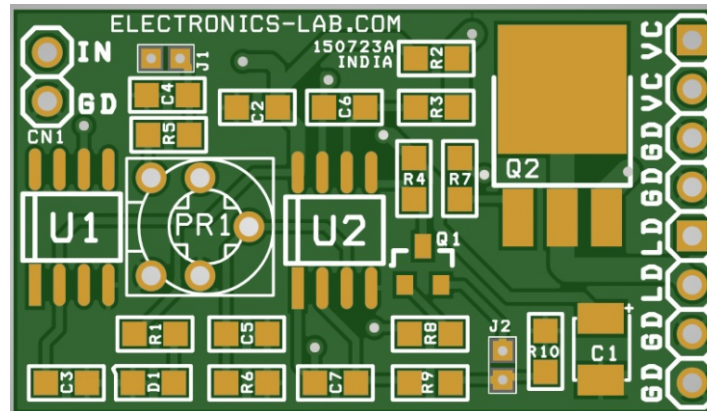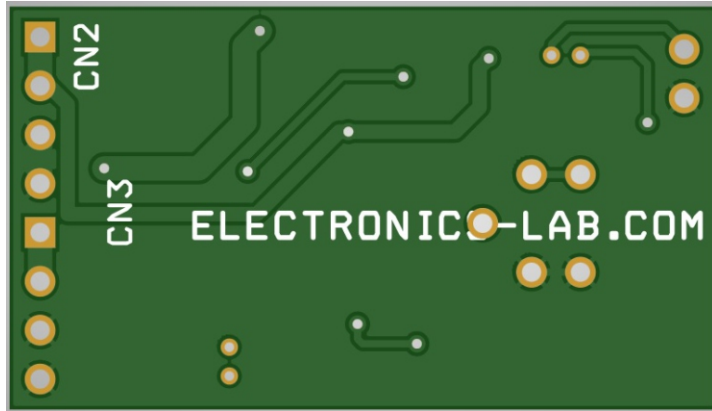

SILK SCREEN TOP

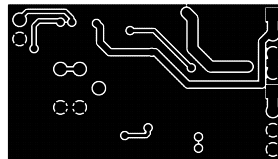

BOTTOM LAYER

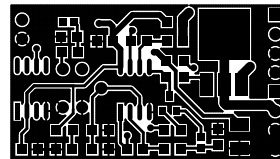

TOP LAYER

PCB DIMENSIONS 36.83 X 20.96MM

Parts List

BOM						
NO	QNTY	REF	DESC	MAUFACTURER	SUPPLIER	SUPPLIER PART NO
1	1	CN1	2 PIN MALE HEADER PITCH 2.54MM	WURTH	DIGIKEY	732-5315-ND
2	2	CN2,CN3	4 PIN MALE HEADER PITCH 2.54MM	WURTH	DIGIKEY	732-5317-ND
3	1	C1	22uF/10V CERAMIC SMD SIZE 1206	YAGEO/MURATA	DIGIKEY	
4	2	C2,C4	100nF/50V CERAMIC SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
5	1	C3	1uF/25V CERAMIC SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
6	1	C5	10PF/50V CERAMIC SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
7	1	C6	2.2nF/50V CERAMIC SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
8	1	C7	1nF/50V CERAMIC SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
9	1	D1	LED SMD SIZE 0805	OSRAM	DIGIKEY	475-1278-1-ND
10	1	J1	JUMPER/PCB SOLDER	PCB-SOLDER	DIGIKEY	
11	1	J2	JUMPER PCB/SOLDER	PCB-SOLDER	DIGIKEY	
12	3	R3,R6,R9	10K 1% SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
13	1	Q1	SI2304DS	NXP	DIGIKEY	2156-SI2304DS215-ND
14	1	Q2	SI2337DS-T1-E3/FDD4685	ON SEMI	DIGIKEY	FDD4685CT-ND
15	2	R1,R4	470E 0.1% SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
16	1	R2	4.7E 0.1% SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
17	1	R5	0E	YAGEO/MURATA	DIGIKEY	
18	1	R7	330E 1% SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
19	1	R8	200E 1% SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
20	1	R10	2K 1% SMD SIZE 0805	YAGEO/MURATA	DIGIKEY	
21	1	U1	REF5020 SOIC8	TI	DIGIKEY	296-22201-5-ND
22	1	U2	OPA2333 SOIC8	TI	DIGIKEY	296-19543-5-ND
23	1	PR1	10K TRIMMER POTENTIOMETER	PIHER	DIGIKEY	1993-PT6KV-103A2020-ND



Keep
In touch..

electronics-lab
.com

info@electronics-lab.com
www.electronics-lab.com

from ideas to **boards**

