



electronics-lab from ideas to boards

electronics-lab - Projects | Embedded News | Online Community | e-Shop

Open Source Hardware Electronics Projects

electronics-lab.com /projects







Lamp Flasher with Timer IC and MOSFET for Automotive Applications



AUTOMOTIVE

Lamp Flasher with Timer IC and MOSFET for Automotive Applications




This is a mini flasher board that can drive high-power LED or a lamp, mainly designed for automotive applications. The project consists BD9555FVM-C timer chip and MOSFET. The circuit is configured as a flasher, and can also be used as a PWM driver with an adjustable duty cycle and frequency. Capacitors C2, R4, and PR1 can be used to set the duty cycle. Please refer to the datasheet of BD9555FVM for more information. N-channel IRF7862 MOSFET used to drive the load, and it's advisable to use maximum load current 3A due to small thermal dissipation on PCB for the MOSFET. The operating power supply is 5V to 15VDC.

FEATURES


- Power Supply 5V to 15V DC
- Load Up to 3Amps
- Flash Frequency 2Hz to 10 Hz
- PWM Frequency range 1Hz to 10Khz (PR1, R4 and C2)
- Adjustable Duty Cycle 1% to 99% (PR1, R4 and C2)
- PCB Dimensions 22.07X10.95MM



Schematic

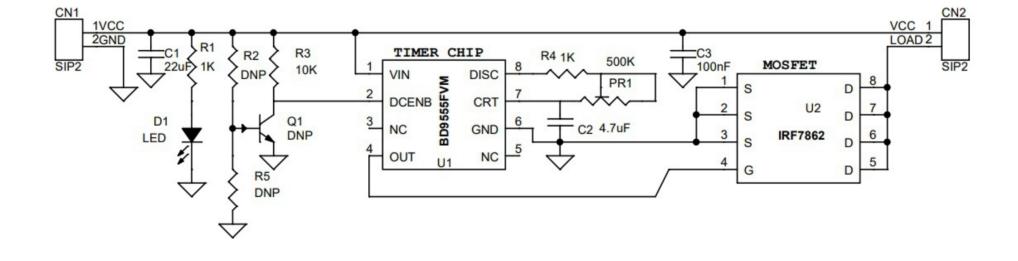


Connections

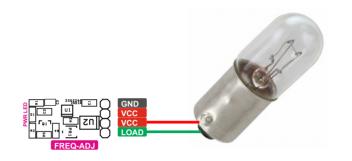


Connections

- CN1: Pin 1 = +DC 5V to 15V, Pin 2 = GND
- CN2: Pin 1 = +DC, Pin 2 = Load
- PR1: Frequency Adjust
- D1: Power LED

PCB

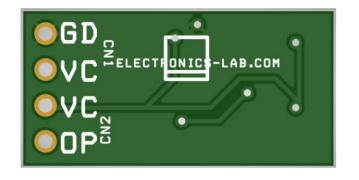

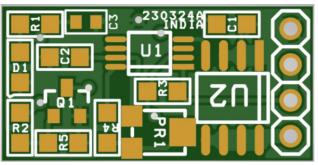









SILK SCREEN TOP

BOTTOM LAYER


TOP LAYER

PCB DIMENSIONS 22.07X10.95MM

Parts List

| вом | | | | | | |
|-----|-------|----------|---------------------------------|--------------|----------|-------------------|
| NO | QNTY. | REF. | DESC. | MANUFACTURER | SUPPLIER | SUPPLIER PART NO |
| 1 | 2 | CN1,CN2 | 2 PIN MALE HEADER PITCH 2.54MM | WURTH | DIGIKEY | 732-5315-ND |
| 2 | 1 | C1 | 22uF/25V CERAMIC SMD SIZE 0805 | YAGEO/MURATA | DIGIKEY | |
| 3 | 1 | C2 | 4.7uF/16V CERAMIC SMD SIZE 0805 | YAGEO/MURATA | DIGIKEY | |
| 4 | 1 | C3 | 100nF/50V CERAMIC SMD SIZE 0805 | YAGEO/MURATA | DIGIKEY | |
| 5 | 1 | D1 | SMD LED SIZE 0805 | OSRAM | DIGIKEY | 475-1278-1-ND |
| 6 | 1 | PR1 | 500K 3MM SMD TRIMMER POT | BOURNS | DIGIKEY | TC33X-2-504ECT-ND |
| 7 | 3 | Q1,R2,R5 | DNP | | | |
| 8 | 2 | R1,R4 | 1K 5% SMD SIZE 0805 | YAGEO/MURATA | DIGIKEY | |
| 9 | 1 | R3 | 10K 5% SMD SIZE 0805 | YAGEO/MURATA | DIGIKEY | |
| 10 | 1 | U1 | BD9555FVM MSOP8 | ROHM | DIGIKEY | BD9555FVM-CGCT-ND |
| 11 | 1 | U2 | IRF7862 SOIC8 | INFINEON | DIGIKEY | IRF7862TRPBFCT-ND |

Notes

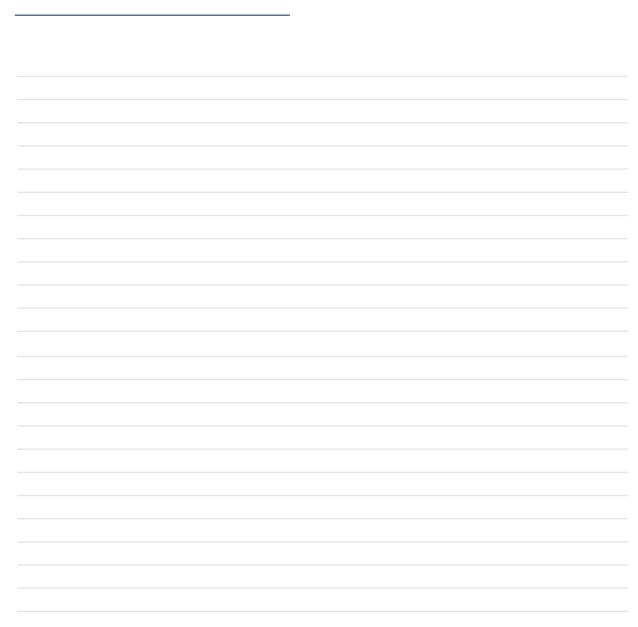



APP

Android App

DOWNLOAD



Android App launched in 2017 and has 100k+downloads - rated with 4.5 stars.

SCAN QR CODE





from ideas to boards











